

Homework 3


Page 95, Chinese textbook

Question 12

Considering a three-phase bridge fully-controlled rectifier circuit under a resistive load, if one thyristor cannot be conducted, what does the rectifier voltage waveform u_d look like? If one thyristor has been broken down and is a short circuit now, what is the influence on the other thyristors?

Solution:

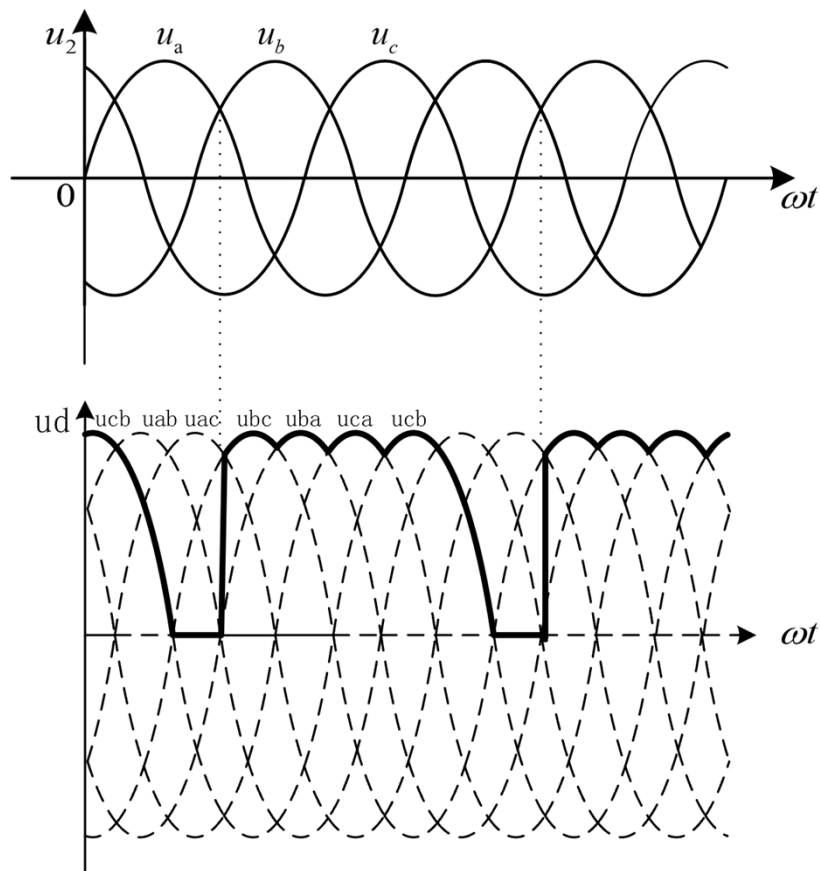Assuming that VT1 could not be conducted, and the firing angle $\alpha=0$, then the waveform of u_d would look like:



If VT1 is broken down and is a short circuit now. When VT3 and VT5 is conducting, a short circuit can be formed between phase a and b or phase a and c. The increasing voltage may cause damage to VT3 and VT5.


Question 13

Considering a three-phase bridge fully-controlled rectifier circuit with $U_2 = 100V$, under a resistive and inductive load with $R = 5\Omega$ and very large inductance, when $\alpha = 60^\circ$:

- 1) Draw the waveform of u_d , i_d and i_{VT1} ;
- 2) Calculate U_d , I_d , I_{dVT} , I_{VT} .

Solution:

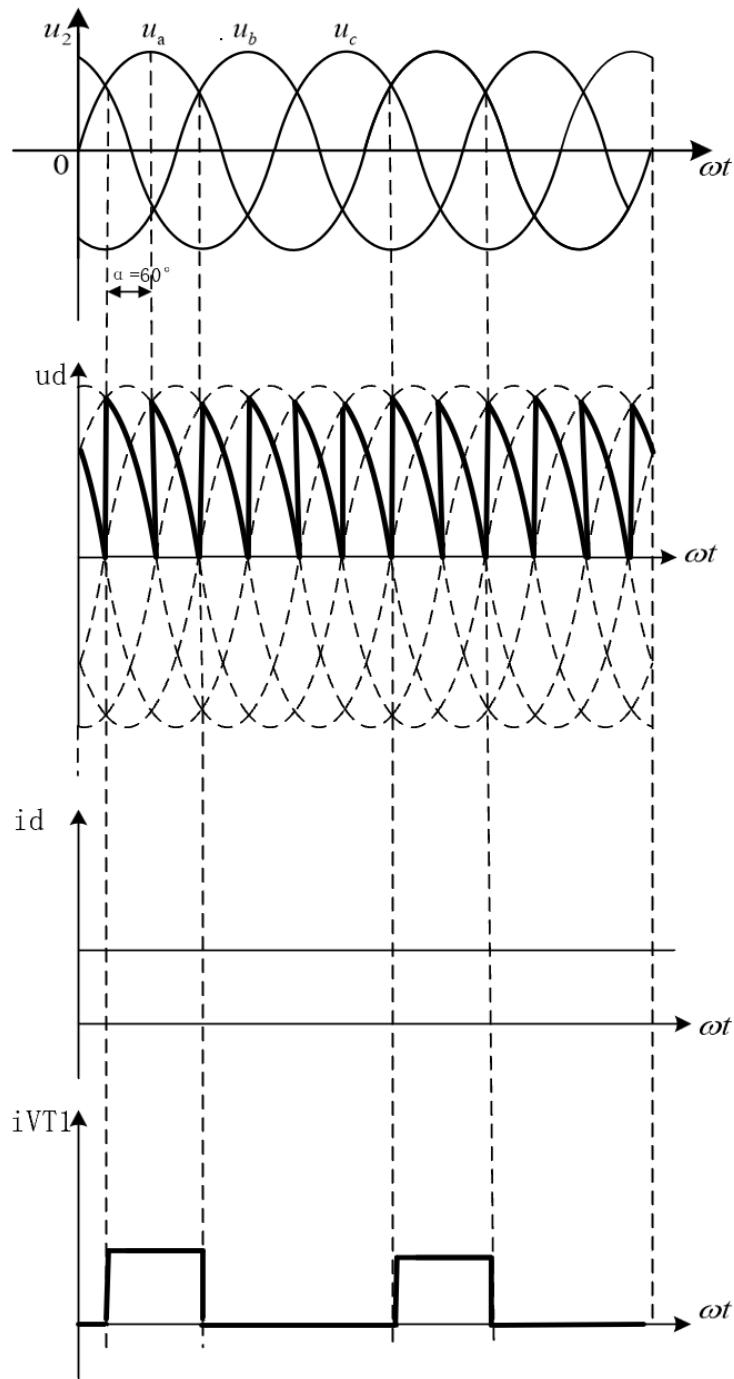1) The waveform of u_d , i_d and i_{VT1} is shown as below:



2)

$$U_d = \frac{3}{\pi} \int_{\alpha + \frac{\pi}{3}}^{\alpha + \frac{2\pi}{3}} \sqrt{6} U_2 \sin \omega t d\omega t = 2.34 U_2 \cos \alpha = 117 (V)$$

$$I_d = \frac{U_d}{R} = 23.4 (A)$$

$$I_{dT} = \frac{1}{3} I_d = 7.8 (A)$$

$$I_{VT} = \frac{1}{\sqrt{3}} I_d \approx 13.51 (A)$$

Question 15

Considering a three-phase half-wave controlled rectifier circuit connected to a EMF load with resistor and inductor, when $U_2 = 100V$, $R = 1\Omega$, $L = \infty$, $L_B = 1mH$, $\alpha = 30^\circ$, $E = 50V$,

calculate the value of U_d , I_d , γ and draw the waveform of u_d , i_{VT1} and i_{VT2}

Solution:

Since this is a three-phase half-wave controlled rectifier, we can see ΔU_d :

$$\Delta U_d = \frac{3X_B I_d}{2\pi}$$

$$X_B = 2\pi f L_B \quad (f = 50Hz)$$

Meanwhile.

$$U_d = 1.17U_2 \cos \alpha - \Delta U_d$$

$$I_d = \frac{U_d - E}{R}$$

Solve these equations:

$$U_d = \frac{3X_B E + \pi R \times 1.17U_2 \cos \alpha}{3X_B + 2\pi R} \approx 94.63(V)$$

$$\Delta U_d = 1.17U_2 \cos \alpha - U_d \approx 6.7(V)$$

$$I_d = 44.63(A)$$


On account of:

$$\cos \alpha - \cos(\alpha + \gamma) = \frac{2I_d X_B}{\sqrt{6} U_2}$$

We can solve γ :

$$\gamma = \arccos(0.752) - 30^\circ \approx 11.24^\circ$$

The waveform of u_d , i_{VT1} and i_{VT2} is shown as below:

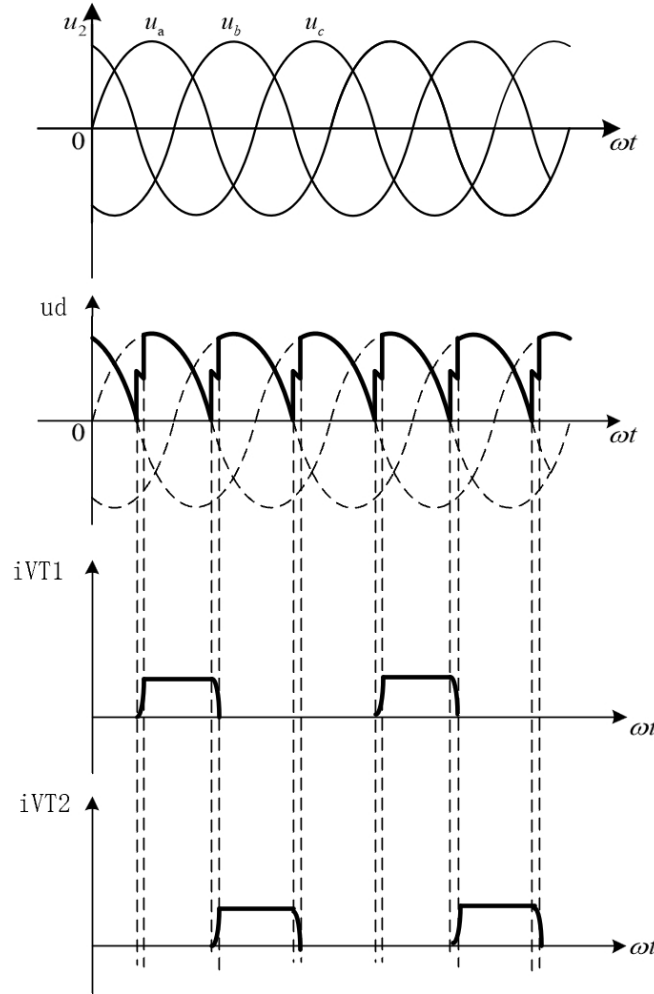

Question 16

Considering a three-phase bridge uncontrolled rectifier circuit connected to a resistive and inductive load, with $R = 2\Omega$, $L = \infty$, $U_2 = 100V$, $X_B = 0.1\Omega$, calculate the value of U_d , I_d , I_{VD} , I_2 , and γ , and draw the waveform of u_d , i_{Vd} , i_{22} .

Solution:

Three-phase bridge uncontrolled rectifier circuit is equal to three-phase bridge fully-controlled rectifier with α being 0.

$$U_d = 2.34U_2 \cos \alpha - \Delta U_d$$

$$\Delta U_d = \frac{3X_B I_d}{\pi}$$

$$I_d = \frac{U_d}{R}$$

We can see:

$$U_d = \frac{2.34U_2 \cos \alpha}{1 + 3X_B/\pi R} \approx 223.37 (V)$$

$$I_d = 111.685 (A)$$

$$I_{VD} = I_d/3 \approx 37.23 (A)$$

$$I_2 = \sqrt{\frac{2}{3}} I_d \approx 91.19 (A)$$


Since:

$$\cos \alpha - \cos(\alpha + \gamma) = \frac{2I_d X_B}{\sqrt{6} U_2}$$

We can solve the commutation angle:

$$\gamma = \arccos\left(1 - \frac{2I_d X_B}{\sqrt{6} U_2}\right) \approx 24.67^\circ$$

The waveform of u_d , i_{Vd} , i_{22} is shown as below:

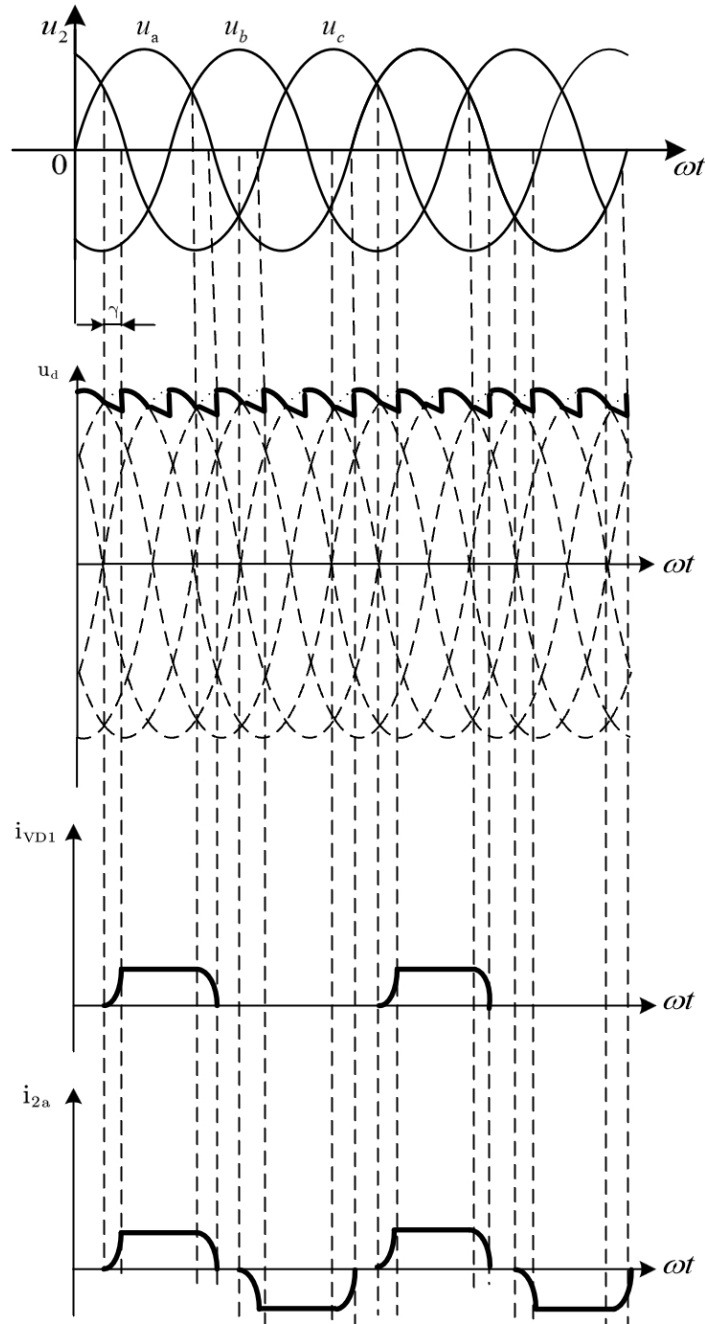

Question 17

Considering a three-phase fully controlled bridge with back electromotive force resistive inductive load, when $E = 200\text{V}$, $R = 1\Omega$, $L = \infty$, $U = 220\text{V}$, $\alpha = 60^\circ$.

- ① $L_B = 0$; ② $L_B = 1\text{Mh}$.

In both cases, calculate the values of U_d and I_d (also calculate γ). Draw the waveforms of u_d and i_{VTr} .

Solution:

1) When $L_B=0$:

$$U_d = 2.34 U_2 \cos \alpha = 257.4 \text{ (V)}$$

$$I_d = \frac{U_d - E}{R} = 57.4 \text{ (A)}$$

2) When $L_B=1\text{Mh}$:

$$U_d = 2.34 U_2 \cos \alpha - \Delta U_d$$

$$\Delta U_d = \frac{3 X_B I_d}{\pi}$$

$$I_d = \frac{U_d - E}{R}$$

We can see:

$$U_d = \frac{3 X_B E + \pi R \times 2.34 U_2 \cos \alpha}{3 X_B + \pi R} \approx 244.15 \text{ (V)}$$

$$I_d = 44.15 \text{ (A)}$$

$$\Delta U_d = 13.25 \text{ (V)}$$


Since:

$$\cos \alpha - \cos (\alpha + \gamma) = \frac{2 I_d X_B}{\sqrt{6} U_2}$$

We can solve the commutation angle:

$$\gamma = \arccos \left(\cos \alpha - \frac{2 I_d X_B}{\sqrt{6} U_2} \right) - \alpha \approx 3.35^\circ$$

The waveform is shown as below:

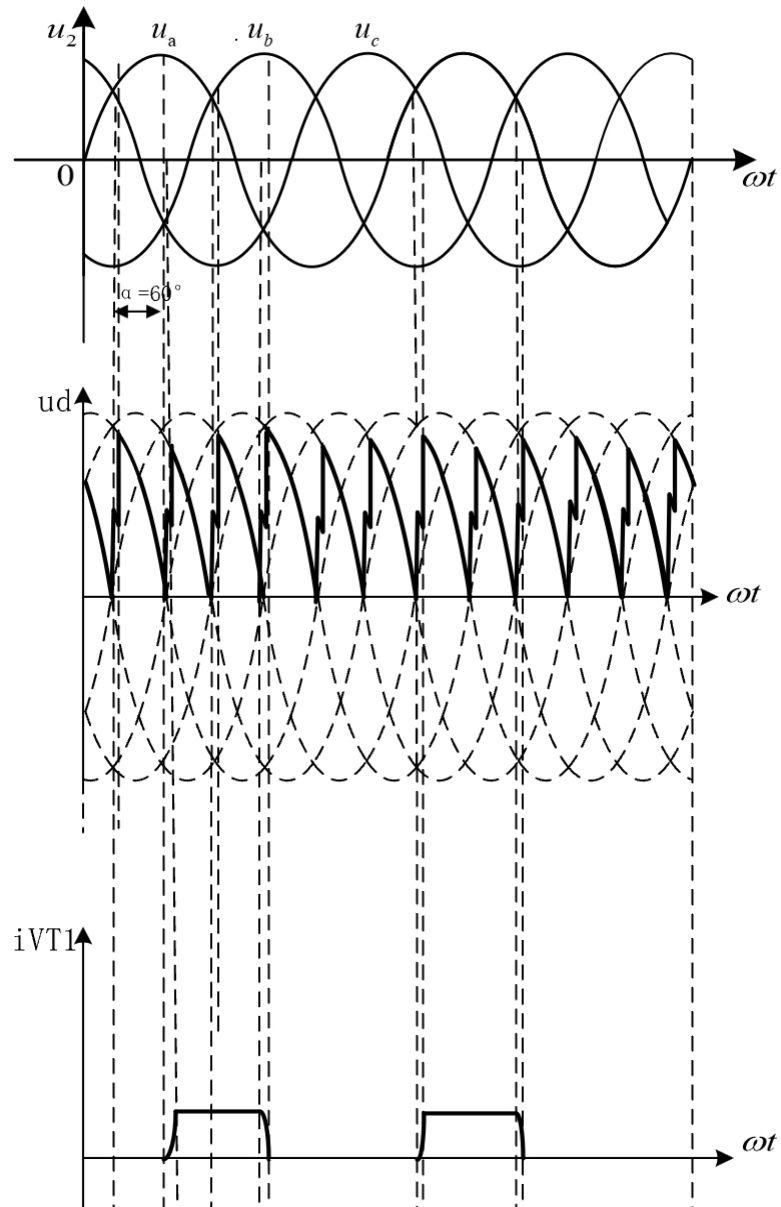

From VT1 to VT6, the latter one's phase is lagged 60° to the former, and the shape of the waveform is totally the same.