

## Homework 2

Page 95, Chinese textbook

### Question 2.1

Figure 3-10 shows a single-phase full-wave controlled rectifier with a transformer center tap.

Is there a problem of dc magnetization in this transformer? Please explain:

- (1) The maximum forward and reverse voltage of the thyristor is  $2\sqrt{2}U_2$
- (2) When the load is a resistor or an inductor, the waveform of the output voltage and current is the same as that of the Single-phase Bridge controlled rectifier.

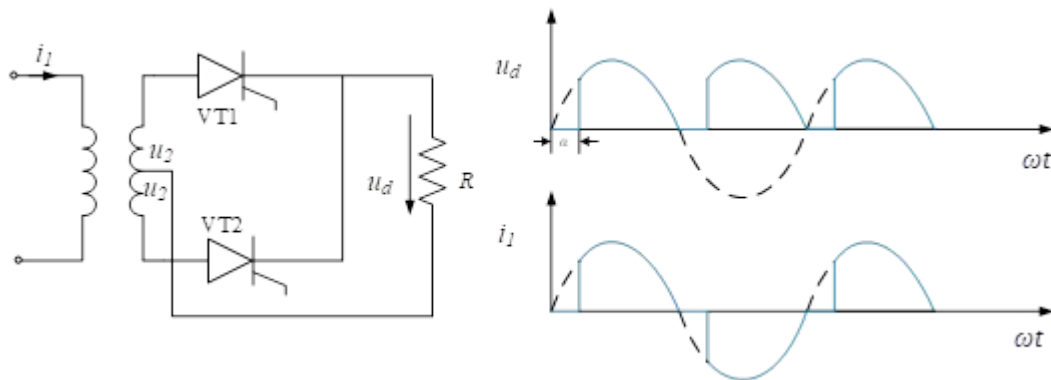



Figure 3-10 Single-phase full-wave controlled rectifier

Answer 2.1


There is no problem of DC magnetization in the transformer. Within a period, the time of the current flowing through the VT1 and VT2 is identical. The magnitude of the current is the same, while the direction is reverse. Therefore, the average value of the current flowing through the transformer equals to 0. So there is no dc magnetization in the transformer.

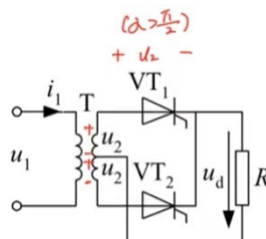- (1) Choose VT1 to be analyzed:

When  $u_2 > 0$ , and VT1 and VT2 are neither conducting. If  $\alpha > \frac{\pi}{2}$ , the maximum forward voltage of the VT1 would be  $\sqrt{2}U_2$  when  $\omega t = \frac{\pi}{2}$ .



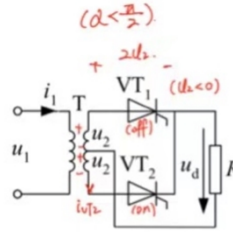When  $u_2 < 0$ , VT2 is conducting and VT1 is off. If  $\alpha < \frac{\pi}{2}$ , the maximum reverse voltage of the VT2 would be  $2\sqrt{2}U_2$  when  $\omega t = \frac{3\pi}{2}$ .



(2) Given that  $\alpha$  in the single phase full-wave rectifier and single-wave bridge fully-controlled rectifier is the same.

When the load is the resistor,  $u_d = i_d \cdot R$ .

$0 < \omega t < \alpha$ : both thyristors are not conducting,  $u_d = 0$ .

$\alpha < \omega t < \pi$ : VT1 is conducting while VT2 is blocked.  $u_d = u_2$ .

$\pi < \omega t < \alpha + \pi$ : VT1 and VT2 are both blocked,  $u_d = 0$ .

$\alpha + \pi < \omega t < 2\pi$ : VT2 is conducting and VT1 is still blocked.  $u_d = -u_2$ .

Therefore, the waveform of  $u_d$  and  $i_d$  is basically identical with that of Single-phase Bridge fully-controlled rectifier with resistive load, which is presented as below.

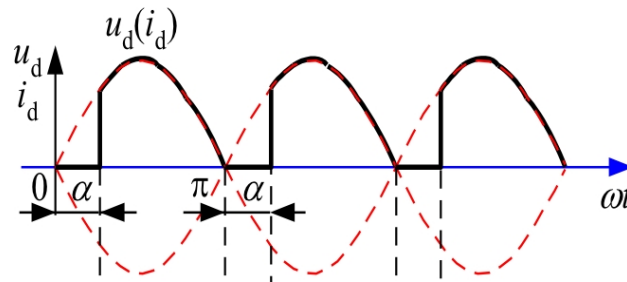


Fig1 The waveform of Single-phase Bridge fully-controlled rectifier with resistive load

When the load is inductive, assuming that the induction is large enough. In this case,  $i_d$  **can be considered as a constant variable**, which also applies to Single-phase Bridge fully-controlled rectifier with large inductive load.

For  $u_d$ :

$0 < \omega t < \alpha$ : VT2 is conducting and VT1 is blocked.  $u_d = -u_2$ .

$\alpha < \omega t < \pi + \alpha$ : VT1 is conducting and VT2 is blocked.  $u_d = u_2$ .

$\pi + \alpha < \omega t < 2\pi$ : VT1 is blocked while VT2 is conducting.  $u_d = -u_2$ .

Hence, the waveform of  $u_d$  is the same as that of Single-phase Bridge fully-controlled rectifier.


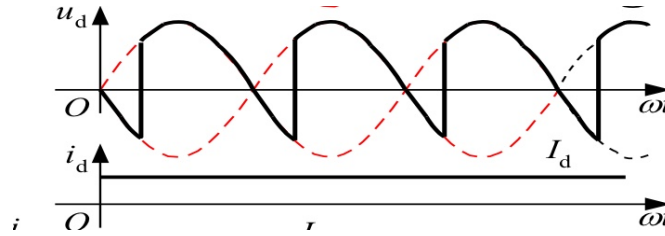


Fig2 The waveform of Single-phase Bridge fully-controlled rectifier with inductive load

### Question 2.2

Single-phase Bridge controlled rectifier,  $U_2=100V$ ,  $R=2\Omega$ , The value of L is very large when  $\alpha = 30^\circ$

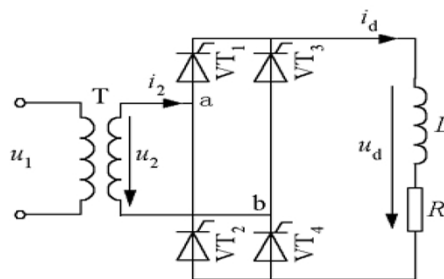- (1) Draw waveform of  $u_d$ ,  $i_d$  and  $i_2$ .
- (2) Compute the rectifier's output average voltage  $U_d$ , current  $I_d$  and RMS value of  $I_2$
- (3) Determine the rated voltage and current of the thyristor considering the safety margin.



### Answer 2.2

- (1) The waveform required ( $\alpha = 30^\circ$ ) is shown as below:

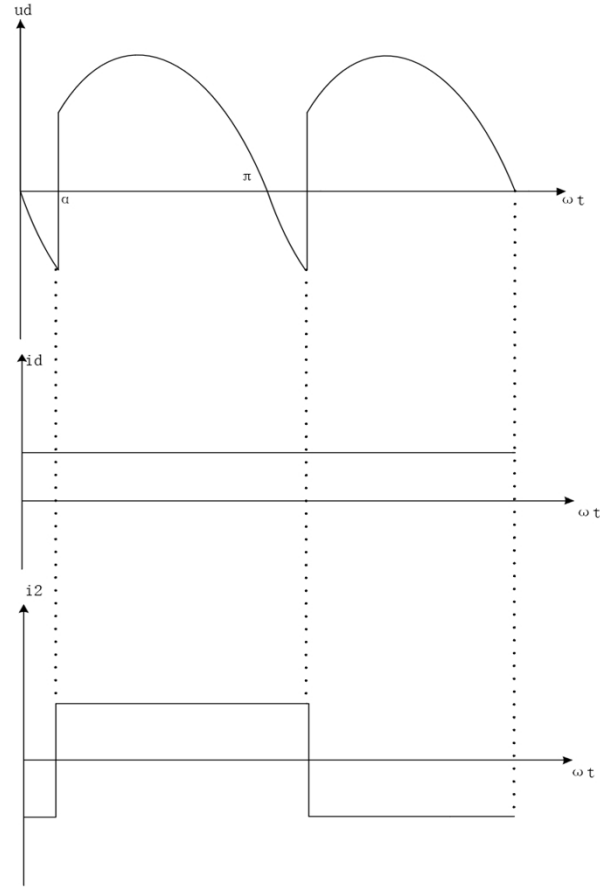


Fig3 The waveform of  $u_d$ ,  $i_d$  and  $i_2$

(2)

$$U_d = 0.9U_2 \cos \alpha = 0.9 \times 100 \times \frac{\sqrt{3}}{2} \approx 77.94V$$

$$I_d = \frac{U_d}{R} = 38.97A$$

$$I_2 = I_d = 38.97A$$

(3) The maximum reverse voltage  $U_{RP}$  of the thyristor would be:

$$U_{RP} = \sqrt{2}U_2 \approx 141.42V$$

The RMS value of the current  $I_{VT}$  flowing through the thyristor would be:

$$I_{VT} = I_d \div \sqrt{2} \approx 27.56A$$

Considering the safety margin, the rated voltage  $U_N$  and rated current  $I_N$  would be:

$$U_N = (2 \sim 3)U_{RP} = 282.84 \sim 424.26V$$

$$I_N = (1.5 \sim 2)I_{VT} \div 1.57 = 26.33 \sim 35.11A$$

### Question 2.3

The circuit of the single-phase bridge half-controlled rectifier circuit in series of thyristors ( $VT_1$  and  $VT_2$  in the bridge are thyristors) is shown in Figure 3-12,  $U_2=100V$ , resistance and inductance load,  $R=2\Omega$ , and  $L$  value is large. When  $\alpha = 60^\circ$ , calculate the effective value of the current flowing through the device, and draw the waveforms of  $u_d$ ,  $i_d$ ,  $i_{VT}$  and  $i_{VD}$ .

### Answer 2.3

The waveform of  $f$   $u_d$ ,  $i_d$ ,  $i_{VT}$  and  $i_{VD}$  is shown as below:

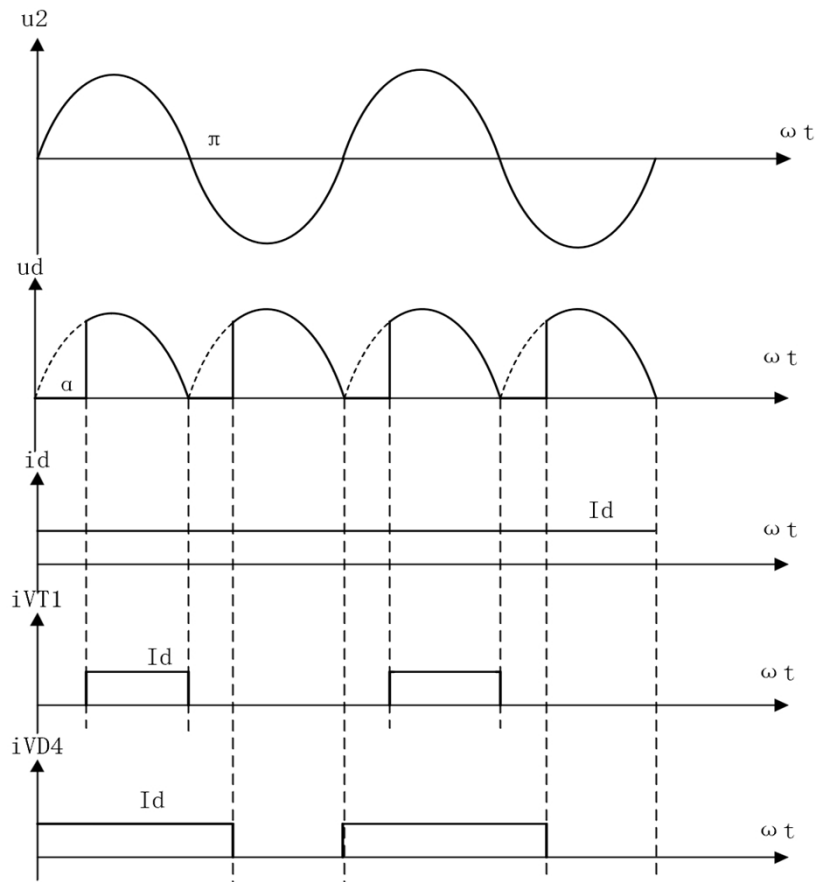


Fig4 The waveform of  $u_2$ ,  $u_d$ ,  $i_{VT}$  and  $i_{VD}$

The average value of  $U_d$  would be:

$$U_d = \frac{1}{\pi} \int_{\alpha}^{\pi} \sqrt{2} U_2 \sin \omega t d(\omega t) = 0.9 U_2 \frac{1 + \cos \alpha}{2} = 67.5 V$$

Then, the average value of  $I_d$  would be:

$$I_d = \frac{U_d}{R} = 33.75 A$$

The effective value of current flowing through thyristor  $I_{VT}$  and diode  $I_{VD}$  would be:

$$I_{VT} = \sqrt{\frac{\int_{\alpha}^{\pi} I_d^2 d\omega t}{2\pi}} = \sqrt{\frac{1}{3}} I_d \approx 19.49 A$$

$$I_{VD} = \sqrt{\frac{\int_0^{\pi+\alpha} I_d^2 d\omega t}{2\pi}} = \sqrt{\frac{2}{3}} I_d \approx 27.56 A$$

#### Question 2.4

Considering a three-phase half-wave controlled rectifier circuit under a resistive or inductive load, respectively, draw the rectifier voltage waveform  $u_d$  when the trigger signal of phase  $\alpha$  disappeared

#### Answer 2.4

Assuming that  $\alpha=0$ , the waveform of  $u_d$  is shown as below:

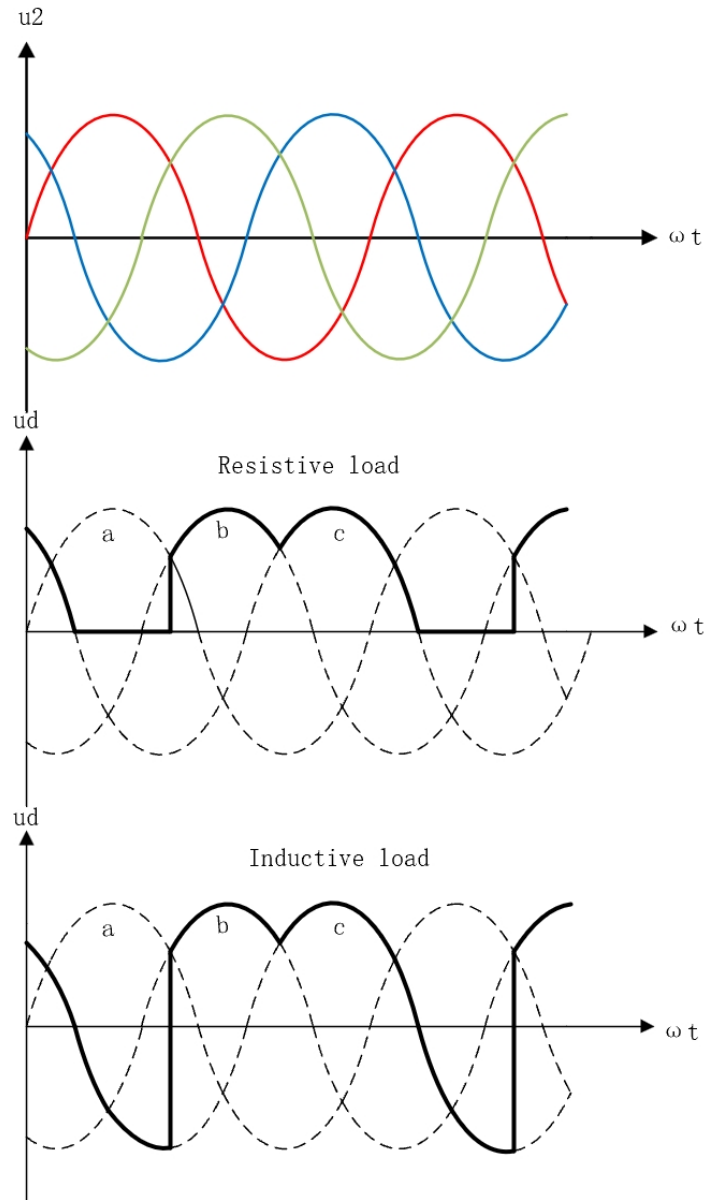


Fig5 The waveform of  $u_d$


### Question 2.5

Considering a three-phase half-wave controlled rectifier circuit with  $U_2=100\text{V}$ , under a resistive and inductive load with  $R=5\Omega$  and very large inductance, when  $\alpha = 60^\circ$ :

- (1) Draw the waveform of  $u_d$ ,  $i_d$  and  $i_{VT1}$  ;
- (2) Calculate  $u_d$ ,  $i_d$  ,  $I_{dVT}$  , and  $I_{VT}$  .

### Answer 2.5

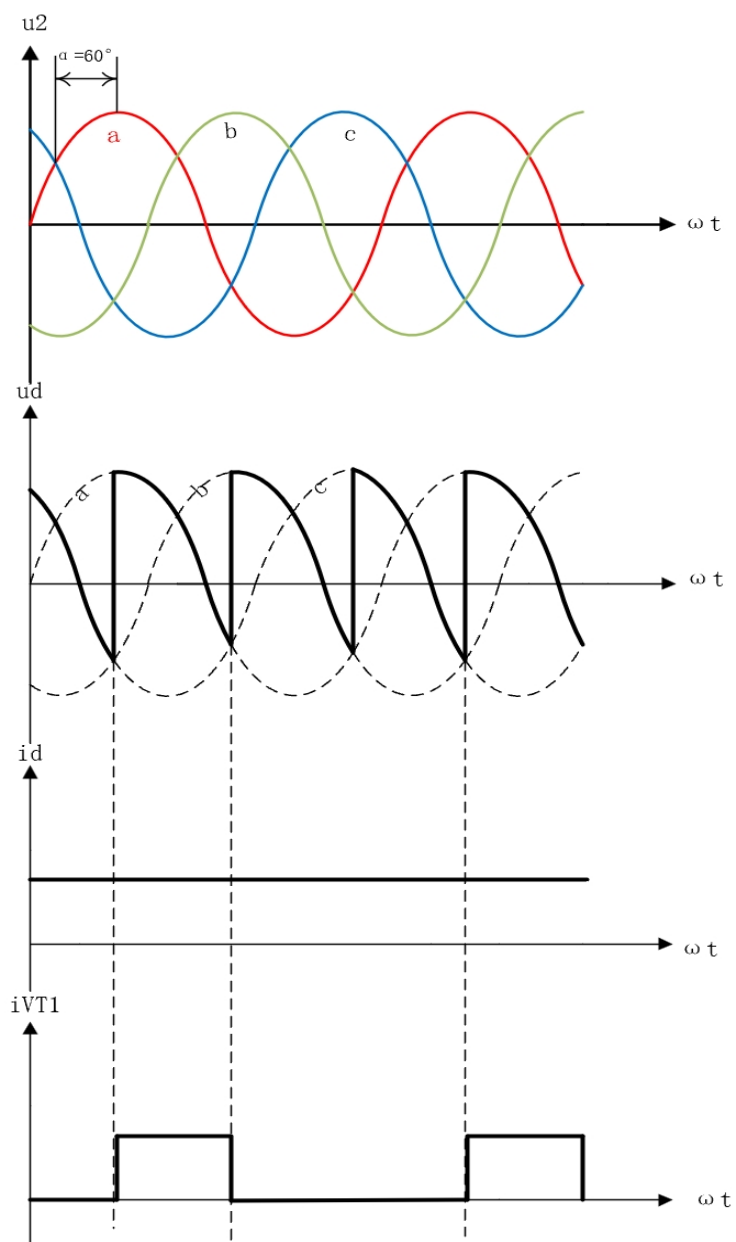(1) The waveform of  $u_d$ ,  $i_d$  and  $i_{VT1}$  is shown as below:



(2)

$$U_d = 1.17 U_2 \cos \alpha = 1.17 \times 100 \times 0.5 = 58.5 V$$

$$I_d = \frac{U_d}{R} = 58.5 \div 5 = 11.7 A$$

$$I_{dVT} = I_d \div 3 = 3.9 A$$

$$I_{VT} = \frac{I_d}{\sqrt{3}} \approx 6.75 A$$